 


## Full\_Adder

### Introduction:

Full Adder is the adder that adds three inputs and produces two outputs. The first two inputs are A and B and the third input is an input carry as C-IN. The output carry is designated as C-OUT and the normal output is designated as S which is SUM. In the following diagram we implement the full adder with the help of two half adders.


### Circuit:




## Code:

Full_adder.V	Testbench
<pre>module Full_adder(a,b,d,s,c); input a,b,d; output s,c; wire x,y,z; xor (x,a,b); xor (s,x,d); and (y,a,b); and (z,x,d); xor(c,z,y); endmodule</pre>	<pre>module Full_adderTB(); reg A,B,D; wire C,S; Full_adder A1(A,B,D,C,S); initial begin A=0; B=0;D=0; #50 A=0;B=0;D=1; #50 A=0;B=1;D=0; #50 A=0;B=1;D=1; #50 A=1;B=0;D=0; #50 A=1;B=0;D=1; #50 A=1;B=1;D=0; #50 A=1;B=1;D=1; #50 \$finish; end initial begin \$display("A, B, D, C, S"); \$monitor(A,"\\t",B,"\\t",D,"\\t",C,"\\t",S); end endmodule</pre>

## Simulation:

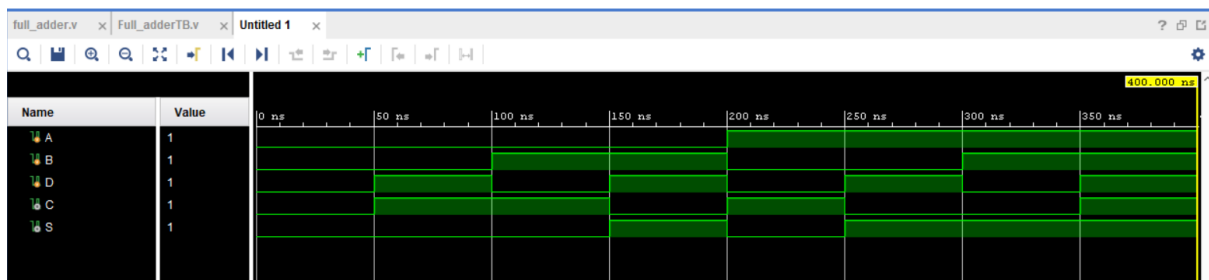

## Elaborate design:

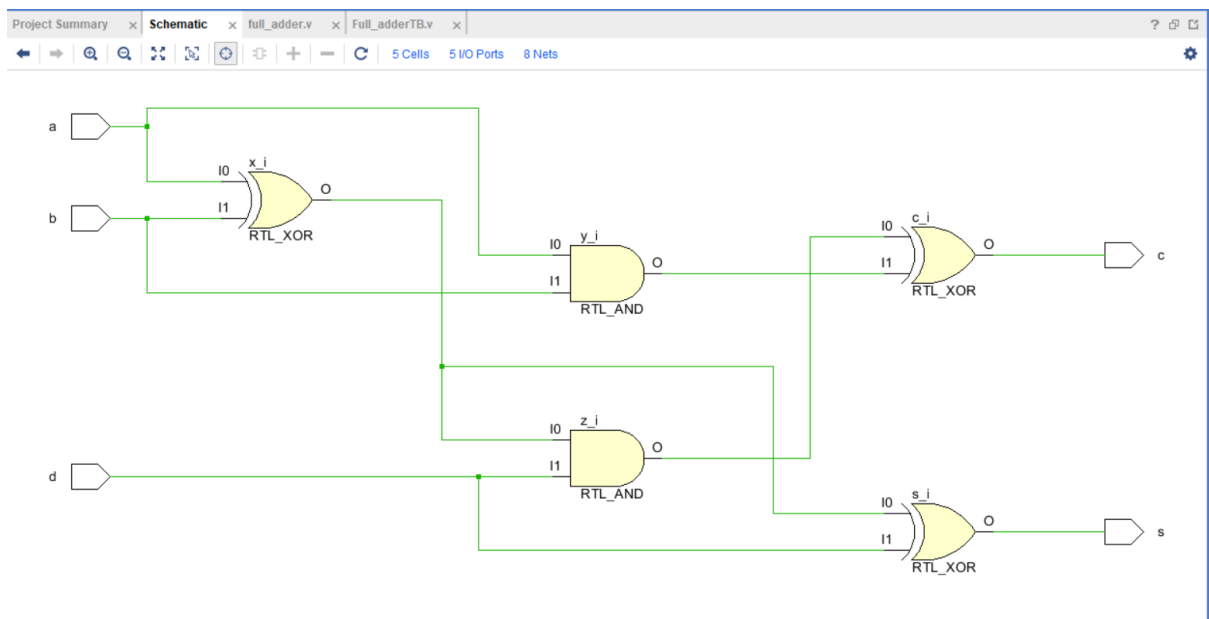

## TCL Console:

```
Tcl Console x Messages Log
# send_msg_id Add_Wave-1 WARNING "No to
# }
# }
# run 1000ns
A, B, D, C, S
0 0 0 0 0
0 0 1 1 0
0 1 0 1 0
0 1 1 0 1
1 0 0 1 0
1 0 1 0 1
1 1 0 0 1
1 1 1 1 1
```